
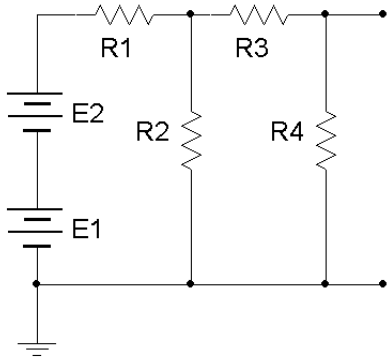


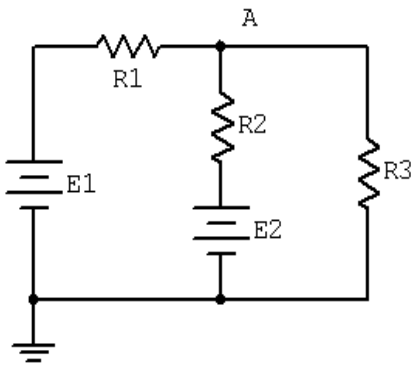1. For the circuit below, find the voltages across R_3 and R_4 . Also find the current through R_1 . $E_1=6V$, $E_2=20V$, $R_1=1k$, $R_2=2k$, $R_3=3k$, $R_4=5k$




2. Solve the circuit below for the voltage across R_3 (i.e., V_A). Do this three ways: A) Convert the sources, combine and solve; B) Use Superposition; C) Create a Thevenin equivalent that drives R_3 and solve. $E_1=10V$, $E_2=20V$, $R_1=1k$, $R_2=2k$, $R_3=3k$.



3. Bonus question: What value of R_3 in problem 2 produces maximum power in R_3 and what is that power?


Answers

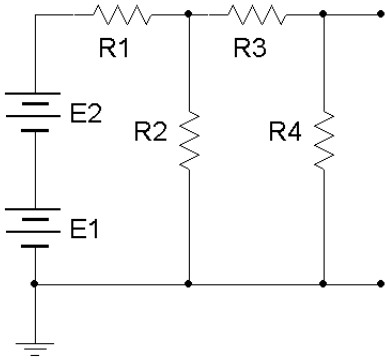1. For the circuit below, find the voltages across R3 and R4. Also find the current through R1. $E_1=6V$, $E_2=20V$, $R_1=1k$, $R_2=2k$, $R_3=3k$, $R_4=5k$



E_1 and E_2 are in series for a total of 26V. One way to find the voltages across R_3 and R_4 is to first find the voltage across R_2 and then perform a voltage divider. The voltage across R_2 can also be found via a voltage divider. The 26V source is split between R_1 (1k) and the combination of R_2 in parallel with the series sum of R_3 and R_4 , or $2k \parallel (3k+5k)=1.6k$. By VDR, V_{R2} is $26V \cdot 1.6k / (1k+1.6k)=16V$. This voltage is then split between R_3 and R_4 . Using VDR again, $V_{R4}=16 \cdot 5k / (5k+3k)=10V$, and by KVL, $V_{R3}=16V-10V$ or 6V. Finally, $V_{R1}=26V-16V$ (from KVL) or 10V. Therefore, $I_{R1}=10V/1k=10mA$.

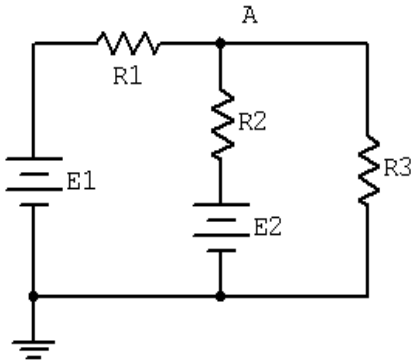2. Solve the circuit below for the voltage across R3 (i.e., V_A). Do this three ways: A) Convert the sources, combine and solve; B) Use Superposition; C) Create a Thevenin equivalent that drives R3 and solve. $E_1=10V$, $E_2=20V$, $R_1=1k$, $R_2=2k$, $R_3=3k$.



A: The first source converts to $10V/1k=10mA$ in parallel with $1k$. The second converts to $20V/2k=10mA$ in parallel with $2k$. This leaves a complete parallel-only circuit consisting of $20mA$ feeding $1k||2k||3k=545.5$. The parallel voltage is $20mA*545.5=10.91V$

B: For superposition, consider each source by itself and replace all other sources with their ideal internal resistance (a short for E sources, an open for I sources). For E1 we wind up with E1 feeding R1 which is in series with the parallel combo of $R_2||R_3$. $R_2||R_3=1.2k$. A voltage divider will yield V_{R3} thusly: $V_{R3}=10V*1.2k/(1k+1.2k)=5.455V$. Considering source E2, we wind up with E2 feeding R2 which is in series with the combo of $R_1||R_3$. $R_1||R_3=750$. A voltage divider yields V_{R3} as follows: $V_{R3}=20V*750/(750+2k)=5.455V$. Both of these potentials are positive with respect to ground so we add them to find the final value of V_{R3} , or $5.455+5.455=10.91V$.

C: For the Thevenin equivalent, unhook R3 and peer into the two remaining ports. Replace the sources with their ideal internal resistances (short the E sources) to find R_{th} . This yields $R_1||R_2$ or 666.7 . E_{th} is the open circuit output voltage which is V_A (with R3 removed, of course). The resulting circuit is a simple series loop. Note that E2 and E1 oppose producing $20V-10V=10V$ with the polarity of E2 (a counterclockwise current). This potential splits between R1 and R2. $V_{R2}=10V*2k/(1k+2k)=6.667V$. Note the polarity of V_{R2} is + to - ground to A. Therefore, $V_A=E_2-V_{R2}$ or $20V-6.667=13.333V$. The Thevenin equivalent is $13.333V$ in series with 666.7 ohms. Apply this to the load (R3) and use VDR to solve for V_{R3} . $V_{R3}=13.333*3k/(3k+666.7)=10.91V$.

3. Use the Thevenin equivalent. R3 is set to R_{th} or 666.7 . The load will see half the Thevenin voltage due to matched resistors. $P=V^2/R$ so $P_{load_max} = (13.333/2)^2/666.7=66.67mW$.