

DC Circuits Introductory Self Test

(answers on second page)

1. A flashlight uses two 1.5 volt batteries in series with a single bulb. If the current drawn by the bulb is 50 mA, determine:
 - A. The effective resistance of the bulb
 - B. The power dissipated by the bulb
 - C. The life of the batteries if they are rated at 1 amp-hour

2. I like toasted bagels. It takes about 4 minutes to properly toast a bagel in my toaster oven. The oven is rated at 1500 watts. If NiMo charges me 11 cents per KWH, determine:
 - A. The energy used to toast the bagel (in KWH)
 - B. The yearly energy cost to toast one bagel per day.
 - C. The current drawn by the oven.

3. A certain chunk of material has a resistance of 100 Ohms. Determine the new resistance if:
 - A. The length is doubled.
 - B. The area is doubled.
 - C. The length and area are both tripled.
 - D. The material is altered so that its resistivity is increased ten fold.

4. An audio amplifier has an efficiency of 50%. The loudspeaker it drives has an efficiency of 10%.
 - A. What is the net efficiency?
 - B. For a loudspeaker output of 2 watts, what power must be drawn by the amplifier?

5. A 60 volt source feeds four series connected resistors. R1 is 100 Ohms, R3 is 500 Ohms, R4 is 200 Ohms. R4 also dissipates .5 watts. Determine:
 - A. The value of R2.
 - B. The voltage drop across each resistor.
 - C. The total power dissipated in the circuit resistors.

DC Circuits Introductory Self Test Answers

1. A. $R=V/I$ $3 \text{ V}/50 \text{ mA} = 60 \text{ Ohms}$
 B. $P=I*V$ $50 \text{ mA} * 3 \text{ V} = 150 \text{ mW}$
 C. $1 \text{ Ah}/50 \text{ mA} = 20 \text{ hours}$

2. $4 \text{ minutes} = 4/60 = .0667 \text{ hours}$
 A. $.0667 \text{ hours} * 1500 \text{ W} = 100 \text{ wH} (.1\text{KWH})$
 B. $365 \text{ days/year} * .1 \text{ KWH/day} = 36.5 \text{ KWH/year}$. At \$.11/KWH, cost = \$4.01
 C. $I=P/V$ $1500 \text{ W}/120 \text{ V} = 12.5 \text{ amps}$

3. Remember: $R=\rho * \text{length}/\text{area}$
 A. R is doubled to 200 Ohms.
 B. R is halved to 50 Ohms
 C. No change, still 100 Ohms
 D. R is 1k Ohms

4. A. $\eta_{\text{net}} = \eta_1 * \eta_2$ $\eta_{\text{net}} = .5 * .1 = .05$ (i.e., 5%)
 B. In other words, 2 watts is 5% of what?
 $P_{\text{in}} = 2 \text{ W} * 1/\eta$ $P_{\text{in}} = 2 \text{ W} * 1/.05$ $P_{\text{in}}=40 \text{ W}$

5. Knowing R_4 and P_{R5} , you can find I: $P=I^2R$, or $I=\sqrt{P/R}$
 $I=\sqrt{.5 \text{ W}/200 \text{ Ohms}}$ $I=50 \text{ mA}$ You can now find the drops on R1, R3, R4.
 $V_{R1}=I*R1$ $V_{R1}=50 \text{ mA} * 100 \text{ Ohms}$ $V_{R1}=5\text{V}$
 $V_{R3}=I*R3$ $V_{R3}=50 \text{ mA} * 500 \text{ Ohms}$ $V_{R3}=25\text{V}$
 $V_{R4}=I*R4$ $V_{R4}=50 \text{ mA} * 200 \text{ Ohms}$ $V_{R4}=10\text{V}$

From KVL, sum of rises must equal sum of drops, so
 $V_{R2}=E - V_{R4} - V_{R3} - V_{R4}$ $V_{R2}=60\text{V} - 5\text{V} - 25\text{V} - 10\text{V}$ $V_{R2}=20\text{V}$

You now know the drop across R2 and the current through it, so
 $R2= V_{R2}/I$ $R2 = 20 \text{ V}/50 \text{ mA}$ $R2 = 400 \text{ Ohms}$

The total power is found using the total voltage applied and the total current drawn:
 $P = I*V$ $P = 50 \text{ mA} * 60\text{V}$ $P = 3 \text{ W}$