
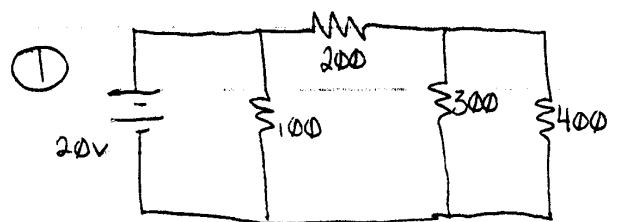


# D.C. Circuit Exercises.


1 of 3

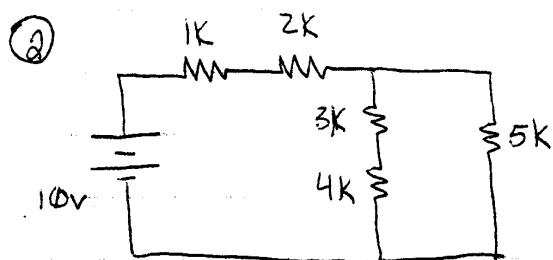


Find  $V_{200}$



Find  $V_{3K}$

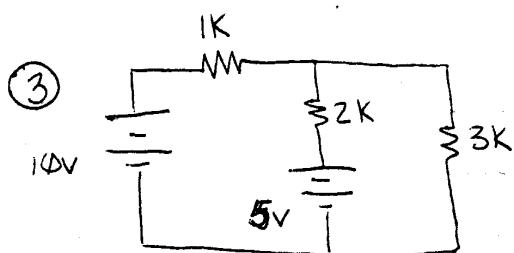

Find  $I_{3K}$

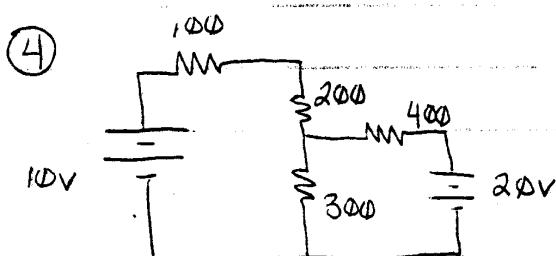


Find  $V_{200}$

# D.C. Circuit Exercises

## Answers

2 of 3


①

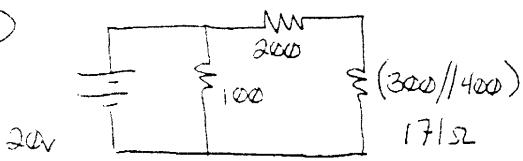


since the  $10\Omega$  is in parallel with the 20V source, it doesn't effect the voltage divider of  $200, 17.1$ .

$$V_{200} = 20V \cdot \frac{200\Omega}{200\Omega + 17.12} = 10.78V$$

②

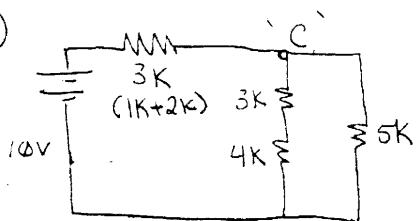

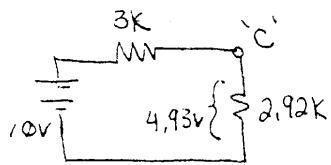
Find  $V_C$  first, Then do a Volt. Div. on  $3K, 4K$ . The  $3K, 4K$  are in series. ( $7K$ ). This result is in parallel with the  $5K$  ( $2.92K$ )



$$V_C = 10V \cdot \frac{2.92K}{3K+2.92K} = 4.93V \quad \text{This voltage divides between the original } 3K \text{ and } 4K.$$

$$V_{3K} = 4.93V \cdot \frac{3K}{3K+4K} = 2.011V$$


③ Superposition.

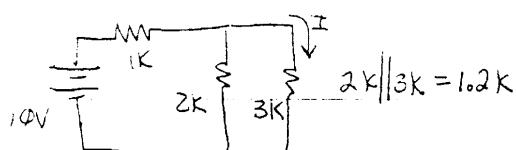


the drop across the  $3K$  for this source is:

$$V_{3K} = 10V \cdot \frac{1.2K}{1.2K+1K} = 5.45V$$
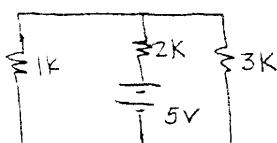
$$I_{3K} = \frac{5.45V}{3K} = 1.82 \text{ mA } (\downarrow)$$



Redraw again!

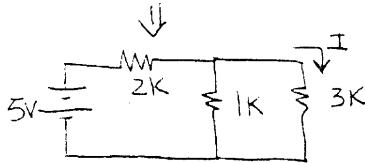

the drop across the  $3K$  for this source is:


$$V_{3K} = 5V \cdot \frac{750\Omega}{2K+750\Omega} = 1.364V$$

$$\text{Result} = 1.82 \text{ mA } (\downarrow) + \frac{1.364V}{3K\Omega} (\downarrow) = 2.275 \text{ mA } (\downarrow)$$


# D.C. circuit EXERCISES.

3 of 3

## (4) Superposition

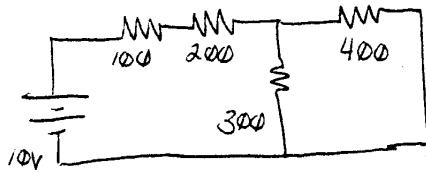


$$300 \parallel 400 = 171\Omega$$

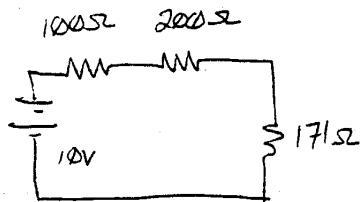


$V_{200}$  for this source is found via voltage divider rule:
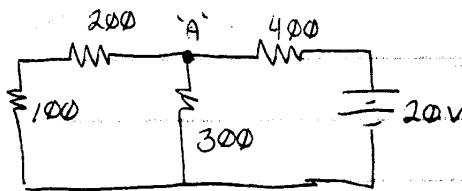
$$V_{200} = 10V \cdot \frac{200}{100 + 200 + 171} = 4.25V (+ -)$$



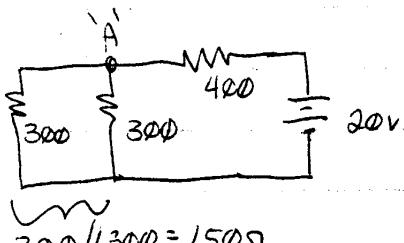If we find  $V_A$ , we can get  $V_{200}$  from the voltage divider rule ( $200, 100$ ).  
100Ω is in series with 200Ω.



$$V_A = 20V \cdot \frac{150\Omega}{150 + 400\Omega} = 5.45V$$

Therefore,  $V_{200} = 5.45V \cdot \frac{200\Omega}{100 + 200}$

$$300 \parallel 300 = 150\Omega$$

$$V_{200} = 3.63V (- +)$$

so, we have two sources "fighting" each other.

The net result is  $4.25V - 3.63V = 0.62V (+ -)$

(or  $\begin{cases} + \\ - \end{cases}$  on the original diagram)