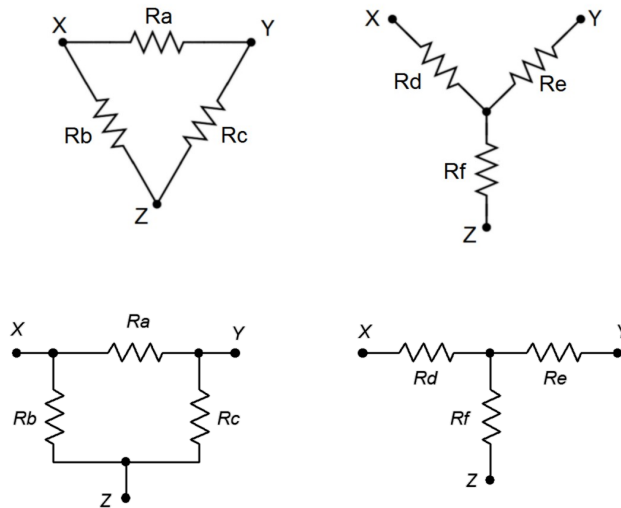


Δ-Y Conversion Proof

Professor Fiore
Mohawk Valley Community College

It is possible to convert a Δ (delta) connected three port network into a Y connected three port network and vice versa. Delta networks are also known as pi networks (both in reference to the Greek letters which mimic the shape of the network), and Y networks are also known as T networks. These are shown below.



A true equivalent circuit would present the same resistance between any two terminals as the original circuit. For the unloaded case, we find:

$$R_{XY} = R_d + R_e = R_a \parallel (R_b + R_c) \quad \text{eq. 1}$$

$$R_{XZ} = R_d + R_f = R_b \parallel (R_a + R_c) \quad \text{eq. 2}$$

$$R_{ZY} = R_e + R_f = R_c \parallel (R_b + R_a) \quad \text{eq. 3}$$

Assuming we have the delta and are looking for the Y equivalent, note that we have three equations with three unknowns (R_d , R_e and R_f). Thus, they can be solved using a term elimination process. If we subtract eq. 3 from eq. 1 we eliminate the second resistance (R_e) and arrive at a difference between the first and third unknown resistances ($R_d - R_f$). This quantity can then be added to eq. 2 to eliminate the third resistance (R_f), leaving just the first unknown resistance (R_d).

$$(R_d + R_e) - (R_e + R_f) = (R_d - R_f) = R_a \parallel (R_b + R_c) - R_b \parallel (R_a + R_c)$$

$$(R_d + R_f) + (R_d - R_f) = 2R_d = 2(R_b \parallel (R_a + R_c) + R_a \parallel (R_b + R_c) - R_c \parallel (R_a + R_b))$$

Therefore,

$$R_d = R_b \parallel (R_a + R_c) + R_a \parallel (R_b + R_c) - R_c \parallel (R_a + R_b)$$

which, after simplifying, is:

$$R_d = R_a R_b / (R_a + R_b + R_c) \quad \text{eq. 4}$$

Similarly,

$$R_e = R_a R_c / (R_a + R_b + R_c) \quad \text{eq. 5}$$

$$R_f = R_b R_c / (R_a + R_b + R_c) \quad \text{eq. 6}$$

Y-Δ Conversion

For the reverse process of converting Y to delta, start by noting the similarities of the expressions for R_d , R_e and R_f . If two of these expressions are divided, a single equation for R_a , R_b or R_c will result. For example, using eq. 4 and 5:

$$R_d / R_e = (R_a R_b / (R_a + R_b + R_c)) / (R_a R_c / (R_a + R_b + R_c)) = R_a R_b / R_a R_c = R_b / R_c$$

Therefore,

$$R_b / R_c = R_d / R_e$$

$$R_b = R_c R_d / R_e$$

This process can be repeated for eq. 4 and 6 to obtain an expression for R_a . The two expressions for R_a and R_b can then be substituted into eq. 4 to obtain an expression for R_c that utilizes only R_d , R_e and R_f . A similar process is followed for R_a and R_b resulting in:

$$R_a = (R_d R_e + R_e R_f + R_d R_f) / R_f$$

$$R_b = (R_d R_e + R_e R_f + R_d R_f) / R_e$$

$$R_c = (R_d R_e + R_e R_f + R_d R_f) / R_d$$