
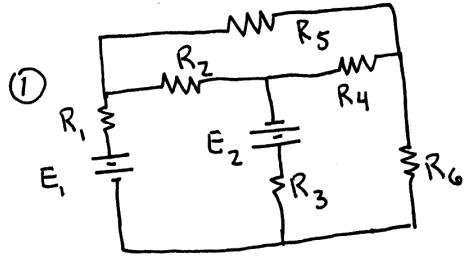


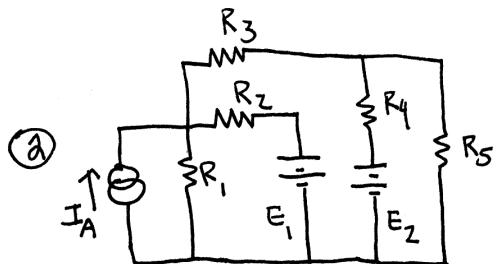
- solve each circuit below using mesh & nodal -



$$\begin{array}{lll} E_1 = 1\text{V} & R_1 = 1\text{k} & R_4 = 4\text{k} \\ E_2 = 2\text{V} & R_2 = 2\text{k} & R_5 = 5\text{k} \\ & R_3 = 3\text{k} & R_6 = 6\text{k} \end{array}$$


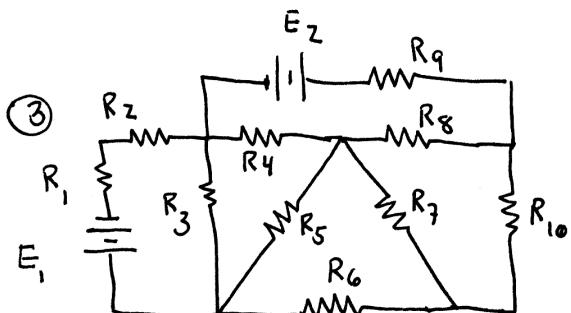
$$\begin{array}{lll} I_A = 5\text{mA} & R_1 = 5\text{k} & R_4 = 2\text{k} \\ E_1 = 5\text{V} & R_2 = 4\text{k} & R_5 = 1\text{k} \\ E_2 = 15\text{V} & R_3 = 3\text{k} & \end{array}$$




$$\begin{array}{lll} E_1 = 6\text{V} & R_1 = 1\text{k} & R_6 = 8\text{k} \\ E_2 = 4\text{V} & R_2 = 3\text{k} & R_7 = 6\text{k} \\ & R_3 = 2\text{k} & R_8 = 5\text{k} \\ & R_4 = 5\text{k} & R_9 = 1\text{k} \\ & R_5 = 4\text{k} & R_{10} = 7\text{k} \end{array}$$



AND NO cookies
until you finish!

① Mesh - format complete

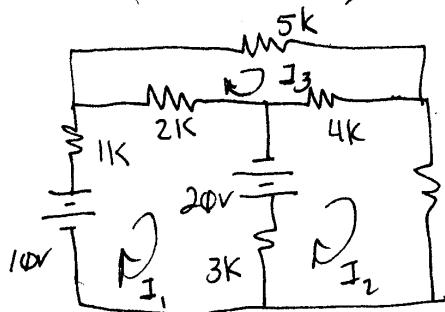

$$\text{Loop 1: } 1\Phi v + 2\Phi v = I_1(1k + 2k + 3k) - I_2 3k - I_3 2k$$

$$\text{Loop 2: } -2\Phi v = -I_1 3k + I_2(3k + 4k + 6k) - I_3 4k$$

$$\text{Loop 3: } \Phi = -I_1 2k - I_2 4k + I_3(2k + 4k + 5k)$$

$$3\Phi = 6kI_1 - 3kI_2 - 2kI_3$$

$$-2\Phi = -3kI_1 + 13kI_2 - 4kI_3$$

$$\begin{matrix} 3\Phi & -3k & -2k \\ -2\Phi & 13k & -4k \\ \Phi & -4k & 11k \end{matrix}$$


$$\text{for } I_1 = \begin{matrix} 6k & -3k & -2k \\ -3k & 13k & -4k \\ -2k & -4k & 11k \end{matrix}$$

$$I_1 = 5.31 \text{ mA}$$

$$I_3 = .959 \text{ mA}$$

$$I_2 = -17.76 \mu\text{A}$$

NODAL - format complete

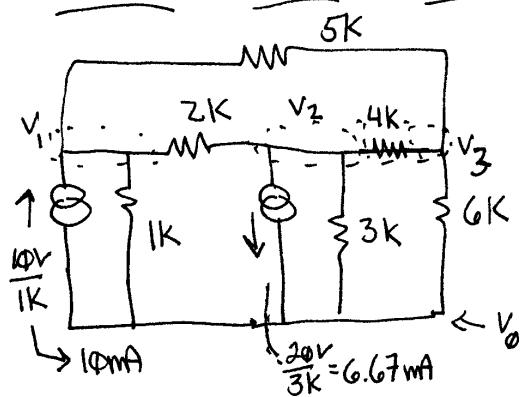

$$\#1: 1\Phi \text{mA} = V_1 \left(\frac{1}{1k} + \frac{1}{2k} + \frac{1}{5k} \right) - V_2 \frac{1}{2k} - V_3 \frac{1}{5k}$$

$$\#2: -6.67 \text{mA} = -V_1 \frac{1}{2k} + V_2 \left(\frac{1}{2k} + \frac{1}{3k} + \frac{1}{4k} \right) - V_3 \frac{1}{4k}$$

$$\#3: \Phi = -V_1 \frac{1}{5k} - V_2 \frac{1}{4k} + V_3 \left(\frac{1}{6k} + \frac{1}{4k} + \frac{1}{5k} \right)$$

$$1\Phi \text{mA} = 1.7E-3 V_1 - .5E-3 V_2 - .2E-3 V_3$$

$$-6.67 \text{mA} = -.5E-3 V_1 + 1.083E-3 V_2 - .25E-3 V_3$$

$$\Phi = -.2E-3 V_1 - .25E-3 V_2 + .6167E-3 V_3$$


$$\begin{matrix} 1.7E-3 & - .5E-3 & - .2E-3 \\ -6.67E-3 & 1.083E-3 & - .25E-3 \end{matrix}$$

$$\text{for } V_1 = \begin{matrix} \Phi & - .75E-3 & .6167E-3 \\ 1.7E-3 & - .5E-3 & - .2E-3 \\ - .5E-3 & 1.083E-3 & - .25E-3 \\ - .2E-3 & - .25E-3 & .6167E-3 \end{matrix}$$

$$V_1 = 4.687V \quad V_3 = -.1097V$$

$$V_2 = -4.02V$$

② Mesh format set up

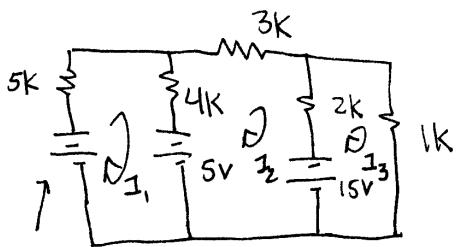

$$5\text{mA} \cdot 5\text{k} = 25\text{V}$$

$$\#1: 25\text{V} - 5\text{V} = I_1(5\text{k} + 4\text{k}) - I_2 4\text{k}$$

$$\#2: 5\text{V} - 15\text{V} = -I_1 4\text{k} + I_2(4\text{k} + 3\text{k} + 2\text{k}) - I_3 2\text{k}$$


$$\#3: 15\text{V} = -I_2 2\text{k} + I_3(2\text{k} + 1\text{k})$$

$$2\phi = 9\text{k}I_1 - 4\text{k}I_2 \quad \phi$$

$$-\phi = -4\text{k}I_1 + 9\text{k}I_2 - 2\text{k}I_3$$

$$15 = \phi - 2\text{k}I_2 + 3\text{k}I_3$$

NODAL format setup

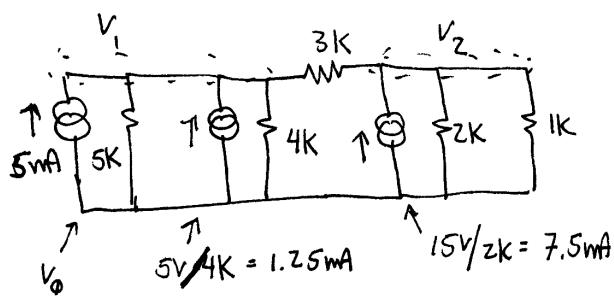


$$\#1: 5\text{mA} + 1.25\text{mA} = V_1 \left(\frac{1}{5\text{k}} + \frac{1}{4\text{k}} + \frac{1}{3\text{k}} \right) - V_2 \left(\frac{1}{3\text{k}} \right)$$

$$\#2: 7.5\text{mA} = -V_1 \frac{1}{3\text{k}} + V_2 \left(\frac{1}{3\text{k}} + \frac{1}{2\text{k}} + \frac{1}{1\text{k}} \right)$$


$$6.25E-3 = .783E-3V_1 - .333E-3V_2$$

$$7.5E-3 = -.333E-3V_1 + 1.833E-3V_2$$

③ NODAL - format setup (PARTIAL)

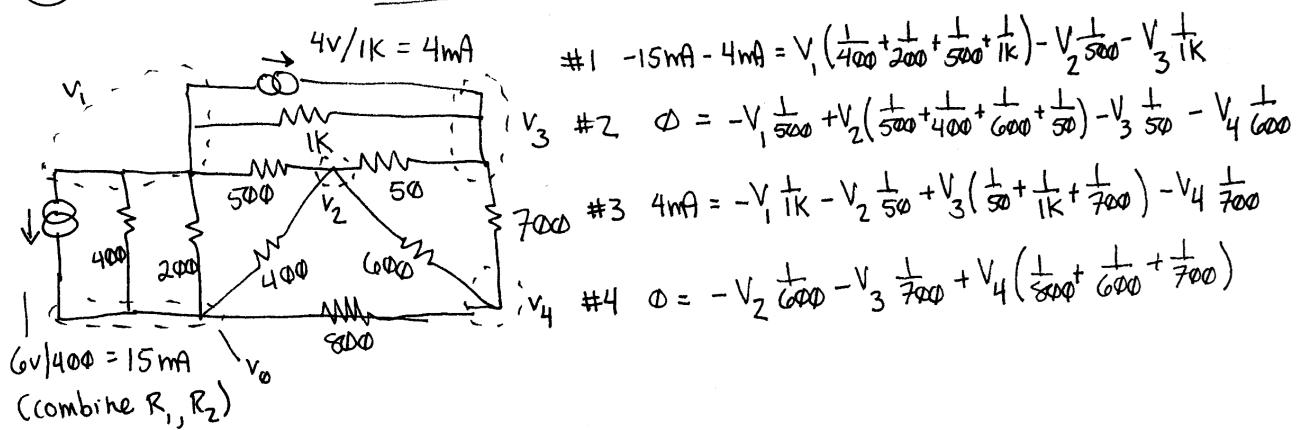

MESH - format setup (PARTIAL)

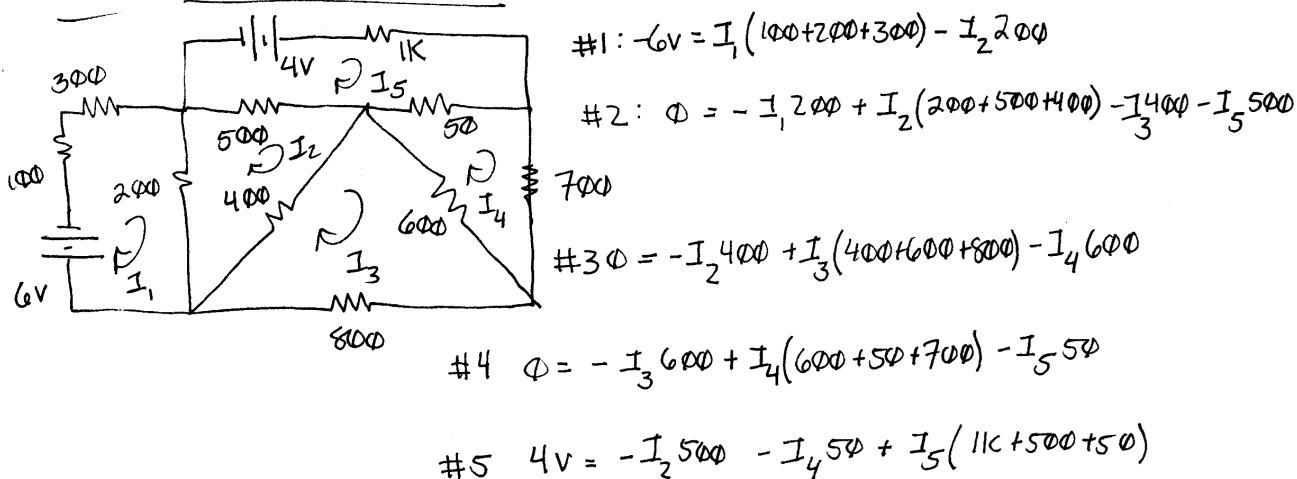

(lots of zero terms!)