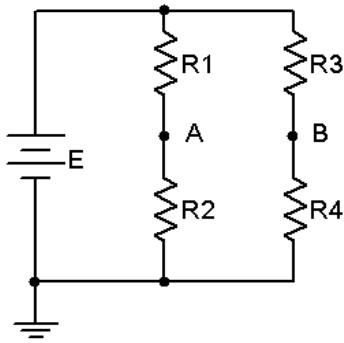



DC Circuits Self Test

Series-parallel, source conversions, Thevenin,
superposition, nodal analysis


1. For the circuit below, find the voltage V_{AB} . Also find the total current exiting the supply. $E=24V$, $R_1=100$, $R_2=200$, $R_3=650$, $R_4=150$



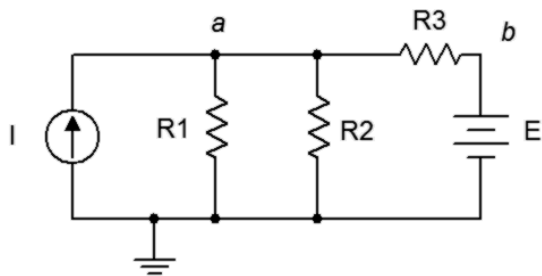
2. Using superposition, solve for the voltage across R_2 . $E=10V$, $I=12mA$, $R_1=3k$, $R_2=6k$, $R_3=2k$. Also, determine the equivalents of the two sources.



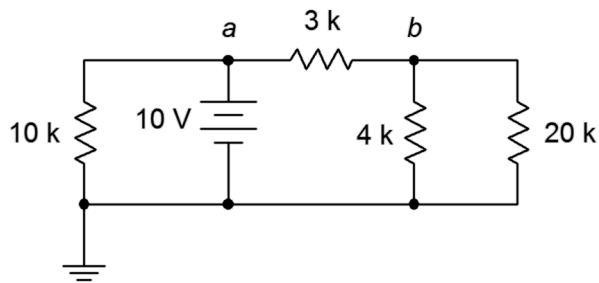3. Find the Thevenin equivalent of the circuit below that drives the $20k$.



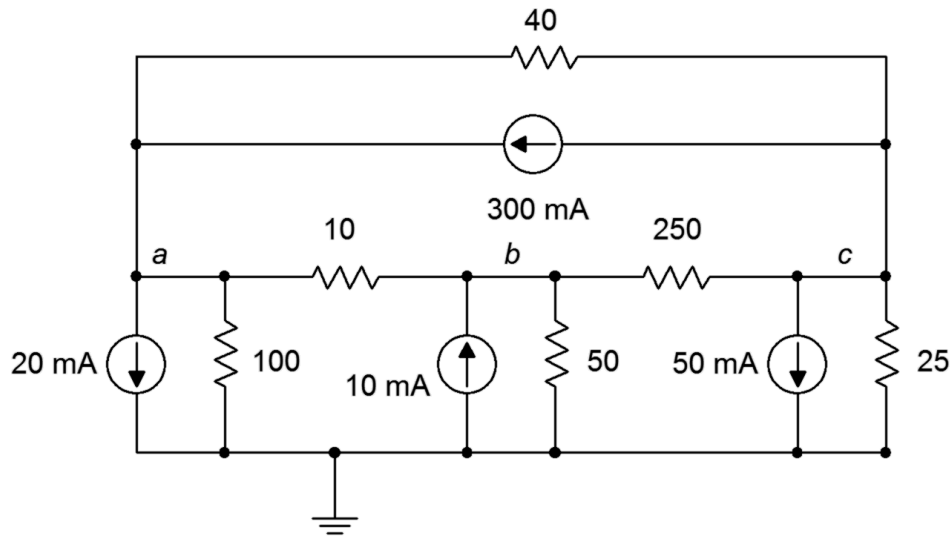4. Using nodal analysis, write the equations for the circuit below. Assume that you compute the resulting node voltages to be: $V_a=1.5V$, $V_b=2.6V$, $V_c=5.9V$. Determine if node B satisfies KCL with these values.



Answers

1. Using voltage dividers, $V_A=24V*200/(100+200)=16V$
 $V_B=24V*150/(150+650)=4.5V$, $V_{AB}=V_A-V_B=16-4.5=11.5V$
 $I=24V/(300||800)=110mA$, or use $16V/200 + 4.5V/150$

2. For the current source, short E. This leaves the three resistors in parallel for $1k$, hence, the voltage across R_2 must be $12mA*1k=12V$ (polarity +/- top to bottom). For the voltage source, open I. This produces a voltage divider between the parallel combo of R_1 and R_2 ($3k||6k=2k$) and R_3 . Thus, the voltage is $10V*2k/(2k+2k)=5V$ (polarity +/- top to bottom). Therefore, the combined total is 17 volts. For source conversion, the current source with R_1 is $12mA*3k=36V$ in series with $3k$. The voltage source with R_3 turns into a current source of $10V/2k=5mA$ in parallel with $2k$.

3. Find the open circuit voltage (b to ground) upon removing the $20k$. Note that the $10k$ will have no impact on this voltage, it is just the divider between the $4k$ and $3k$ for $5.71V$. To find the Thevenin resistance, short the source and look in from the position of the $20k$. Once again the $10k$ has no effect as it is shorted by the source. The result is the parallel combo of the $3k$ and $4k$ for $1.71k$.

4. As this uses just current sources, format nodal may be used:

$$A: 300mA-20mA = (1/100+1/10+1/40)V_A - (1/10)V_B - (1/40)V_C$$

$$B: 10mA = -(1/10)V_A + (1/10+1/50+1/250)V_B - (1/250)V_C$$

$$C: -50mA-300mA = -(1/40)V_A - (1/250)V_B + (1/40+1/250+1/25)V_C$$

Inspecting node B using KCL, incoming currents are the $10mA$ source and the current through the 250 ohm resistor which is $(5.9V-2.6V)/250=13.2mA$, for $23.2mA$ total incoming. Exiting currents are through the 50 ohm which is $2.6V/50=52mA$, and through the 10 ohm which is $(2.6V-1.5V)/10=110mA$, for $162mA$ total. These totals do not match and thus these voltages are not correct.