

CIRCUITS II

"How To Have fun on the weekends"

① Write the expressions for the following waveforms:

- (A) 2 volt peak sinewave at 2 kHz
- (B) 10 volt RMS sinewave at 1 kHz
- (C) 10 volt peak-peak sinewave at 1 kHz, lagging by 90° .
- (D) 5 volt peak sinewave at 100 Hz riding on a +2V DC offset.

② Plot waveform 1-A as seen on a 'scope with the following settings (assume ground is centered and the trigger level and slope are set to start the trace as the waveform passes through 0, going positive).

- (A) vertical: 1v/div, Horizontal: 100 μ sec/div, coupling: AC
- (B) vertical: .2v/div, Horizontal: 200 μ sec/div, coupling: DC

③ Plot waveform 1-D as seen on a 'scope with the following settings (assume ground is centered, Trigger slope is negative, trigger level is approx +1v).

- (A) vertical: 2v/div, Horizontal: 2msec/div, coupling: DC
- (B) vertical: 2v/div, Horizontal: 2msec/div, coupling: AC

④ Find X_L if $f = 1\text{kHz}$, $L = 1\text{mH}$

⑤ Find X_C if $f = 100\text{Hz}$, $C = .1\mu\text{F}$


⑥ Find Z for a series combo of $R = 1\text{k}\Omega$, $L = 10\text{mH}$, if $f = 20\text{kHz}$

CIRCUITS II

2 of 2


"How to have fun on the weekends"

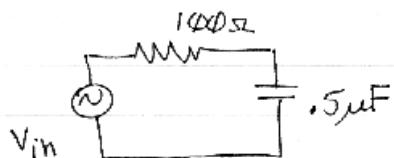- ⑦ Draw the 3 voltage waveforms for the circuit below. (V_{in} , V_R , V_c).
Also, determine total power dissipated.









$V_{in} = 5\text{V peak at } 1\text{kHz}$

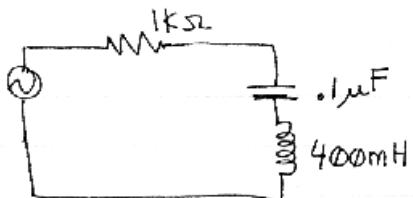- ⑧ Draw the 4 voltage waveforms for the circuit below. (V_{in} , V_R , V_L , V_c)



$V_{in} = 1\text{VOLT at } 500\text{Hz}$

- ⑨ find the frequency for the circuit of problem 8 such that $X_L = X_C$, and determine Z of the circuit at that point.

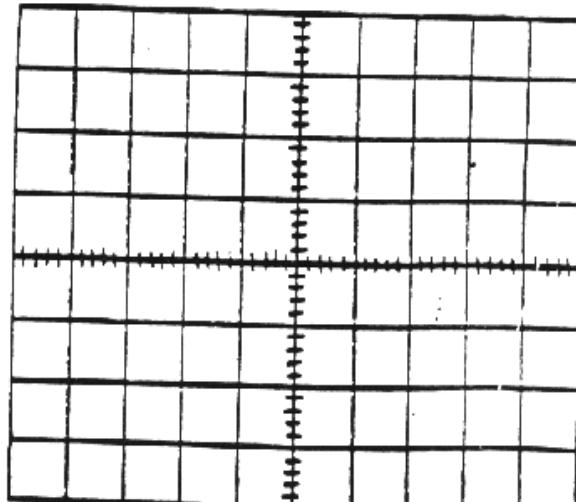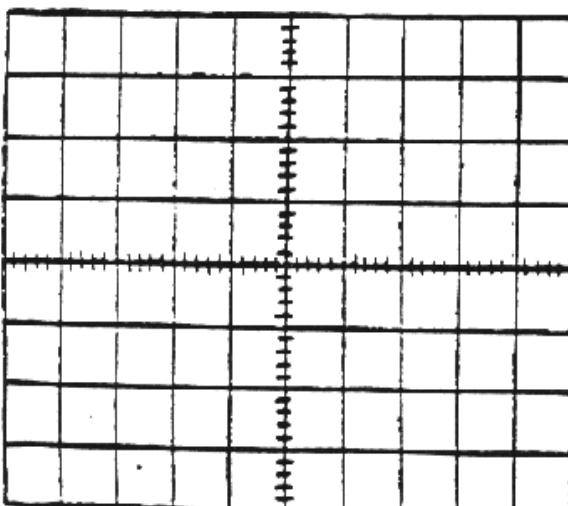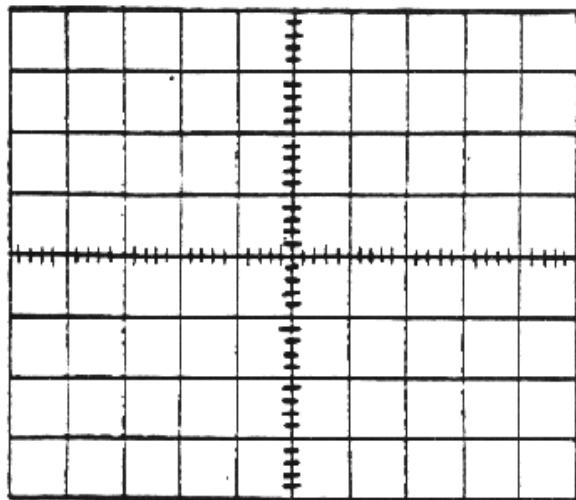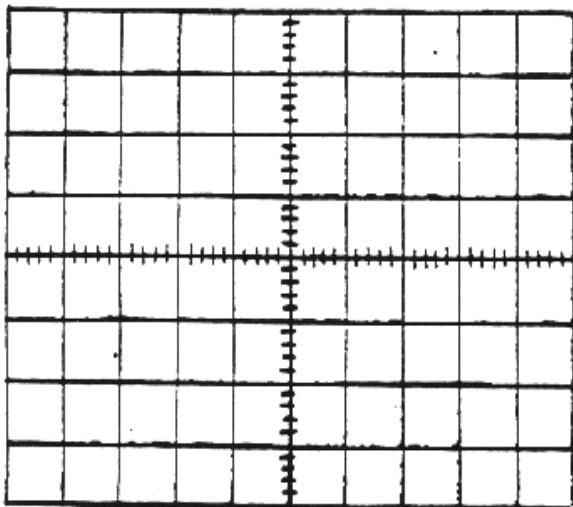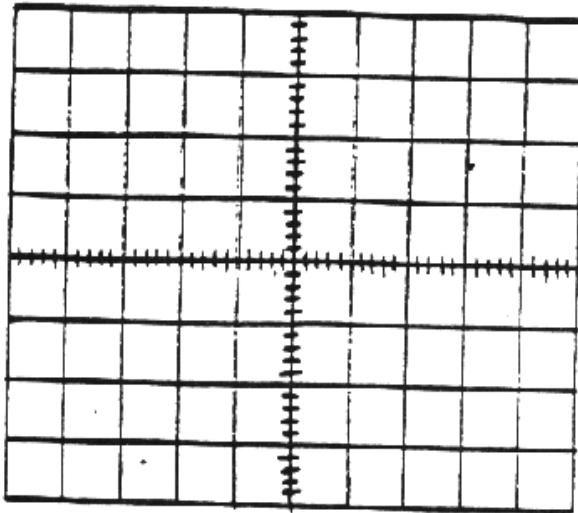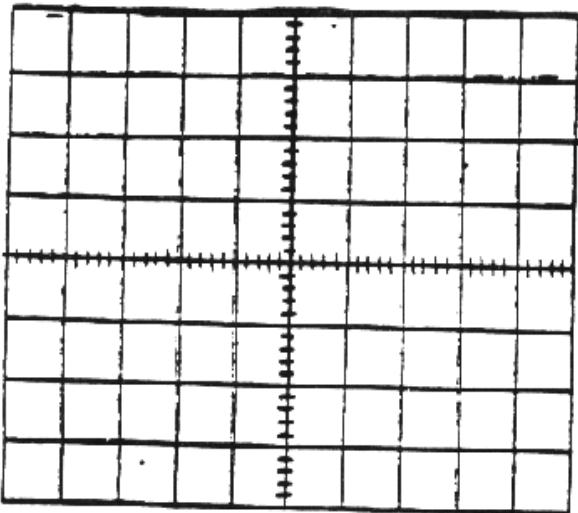

CIRCUITS II

so much weekend fun (answers)

- ① A $v(t) = 2 \sin 2\pi 2000t$
 B $10V \text{ RMS} = 14.14 V \text{ peak}, v(t) = 14.14 \sin 2\pi 1000t$
 C $14V_{pp} = 5V_p, v(t) = 5 \sin(2\pi 1000t - 90^\circ)$
 D $v(t) = 5 \sin 2\pi 1000t + 2$ (note lack of parenthesis for sin)
 or $v(t) = 2 + 5 \sin 2\pi 1000t$ (less confusing)

② + ③ - see graphs

$$④ X_L = 2\pi f L = 2\pi 1\text{kHz} \cdot 1\text{mH} = 6.28 \Omega$$

$$⑤ X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi 100\text{Hz} \cdot 1\mu\text{F}} = 15.9 \text{k}\Omega$$

$$⑥ X_L = 2\pi 20\text{kHz} \cdot 10\text{mH} = 1256 \Omega$$

$$Z = 1k + j 1256 \Omega = 1600 \angle 51.5^\circ \Omega$$


$$⑦ X_C = \frac{1}{2\pi 1\text{kHz} \cdot 5\mu\text{F}} = 318 \Omega$$

$$Z = 1\text{k} - j 318 \Omega = 333.3 \angle -72.6^\circ \Omega$$

$$i = \frac{5 \angle 0^\circ}{333.3 \angle -72.6^\circ \Omega} = 15 \angle 72.6^\circ \text{ mA}$$


$$v_f = 100 \cdot 15 \angle 72.6^\circ \text{ mA} = 1.5 \angle 72.6^\circ \text{ V}$$
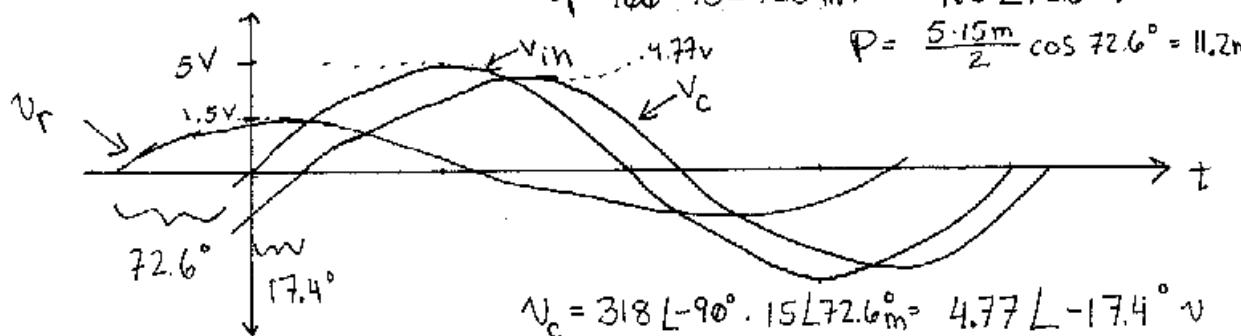
$$P = \frac{5 \cdot 15}{2} \cos 72.6^\circ = 11.2 \text{ mW}$$




Fun so much weekend fun - Circuits II

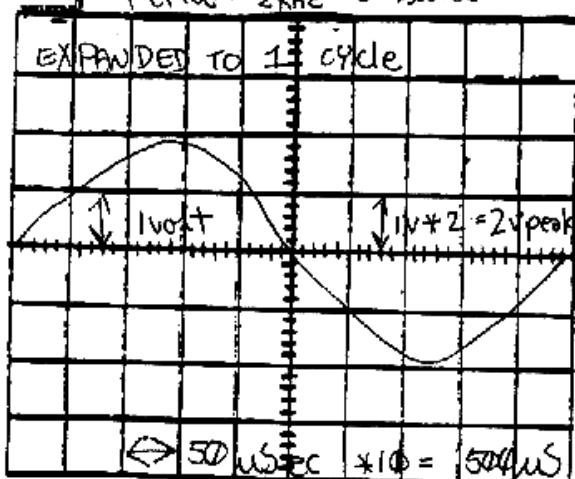
(2A) Period = $\frac{1}{2\text{kHz}} = 500\mu\text{Sec}$



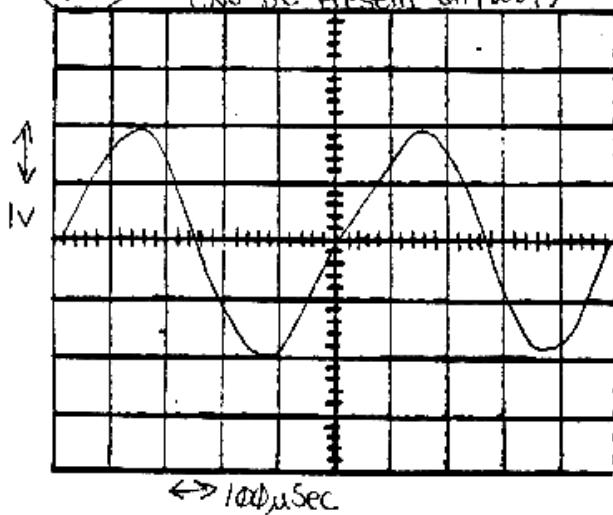
(2A) AC coupling Removes DC
(No DC Present anyway)



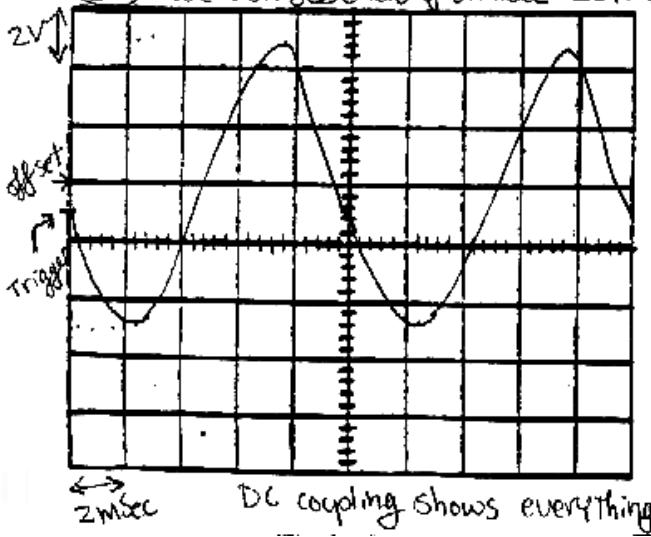(3A) we can see a total of $20\text{msec} = 2$ cycles




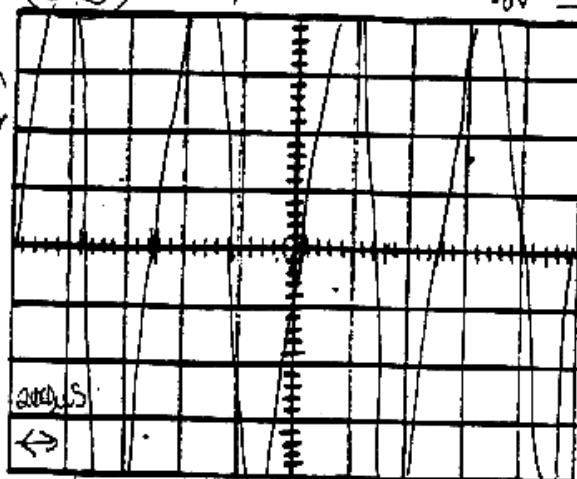(2B) At $.2V/\text{Div}$ we can only see $.8V$




At 2msec , we can see 4 cycles

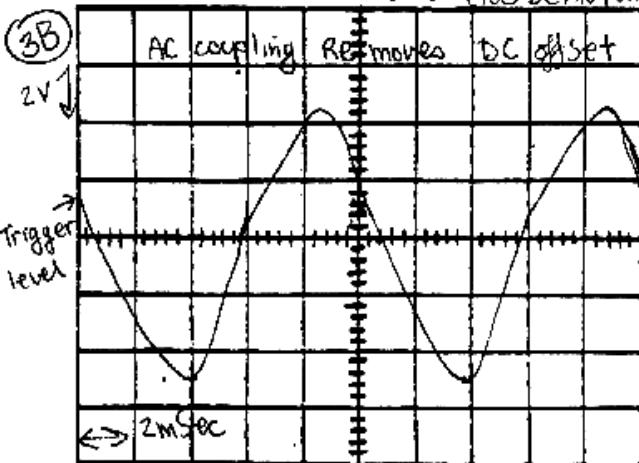DC coupling lets us see both
AC + DC (No DC ANYWAY)



(3B) AC coupling Removes DC offset
— USING SAME TRIGGER AS (2A + 2B)

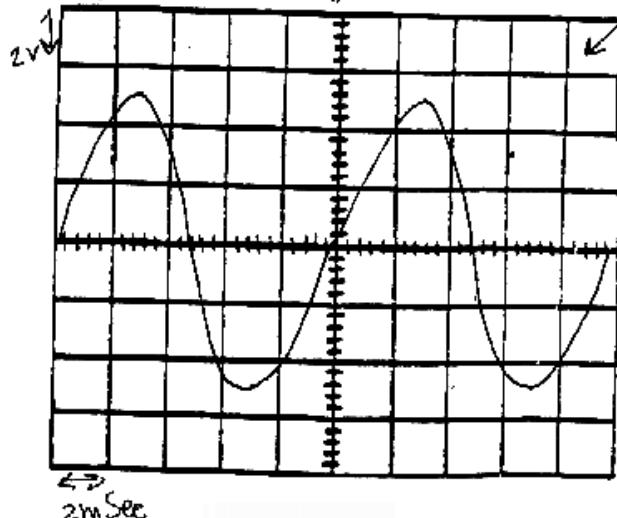

CIRCUITS II

so much fun on the weekends fun (answers, cont.)

$$\textcircled{3} \quad X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi 500 \cdot 1\mu F} = 3185 \Omega$$

$$X_L = 2\pi f L = 2\pi 500 \cdot 400 \text{ mH} = 1256 \Omega$$


$$Z = 1k + j1256 - j3185 \Omega = 1k - j1929 \Omega = 2173 \angle -62.6^\circ \Omega$$

$$I = \frac{140^\circ v}{2173 \angle -62.6^\circ \Omega} = .46 \text{ mA } L62.6^\circ \text{ (current leads voltage - circuit is basically capacitive).}$$

$$V_r = 1k \cdot .46 \text{ mA } L62.6^\circ = .46 \text{ V } L62.6^\circ$$

$$V_c = 3185 \angle -90^\circ \cdot .46 \text{ mA } L62.6^\circ = 1.47 \angle -27.4^\circ \text{ V}$$
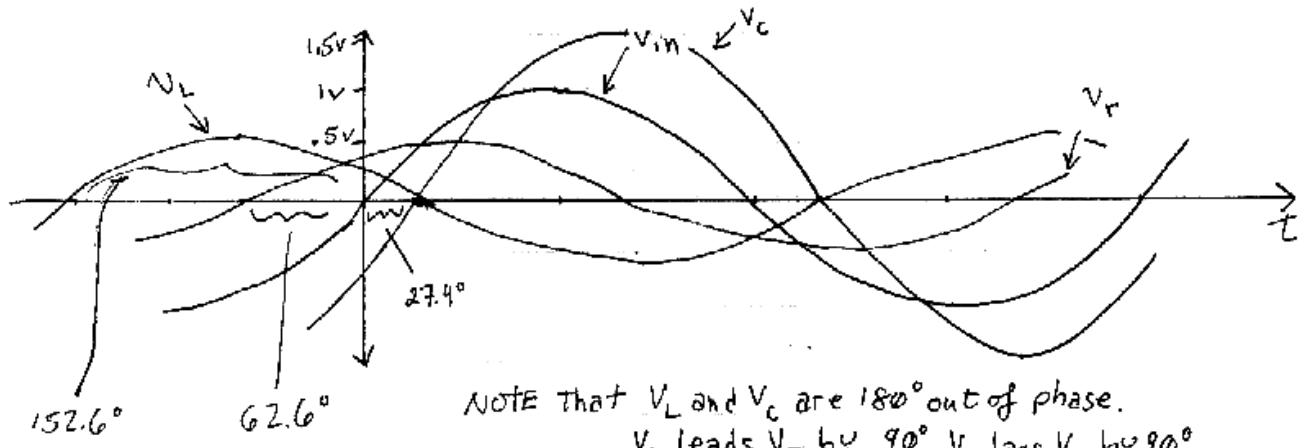
$$V_L = 1256 \angle 90^\circ \cdot .46 \text{ mA } L62.6^\circ = .578 \angle 152.6^\circ \text{ V}$$



NOTE that V_L and V_c are 180° out of phase.
 V_L leads V_r by 90° , V_c lags V_r by 90°

\textcircled{9} since $X_L = 2\pi f L$ and $X_C = \frac{1}{2\pi f C}$, if $X_C = X_L$ then

$$2\pi f L = \frac{1}{2\pi f C}, \quad f^2 = \frac{1}{2\pi C 2\pi L}$$

$$f = \frac{1}{2\pi \sqrt{LC}} \quad f = \frac{1}{2\pi \sqrt{1\mu F \cdot 400 \text{ mH}}} = 796 \text{ Hz}$$

$$X_L = 2\pi 796 \cdot 400 \text{ mH} = 2k\Omega \quad X_C = \frac{1}{2\pi 796 \cdot 1\mu F} = 2k\Omega$$

$$Z = 1k\Omega + j2k - j2k = 1k\Omega$$