
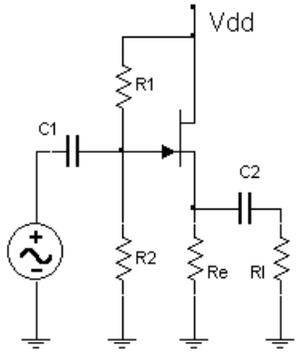


“How many JFETs could Jay fit if JFETs could fit, Jay?”

For the circuits below, find their voltage gain and input impedance. Assume  $V_{DD}=30V$ ,  $I_{DSS}=16mA$  and  $V_{GS(off)}=-4V$  for all circuits. For circuit 1 top left,  $R_1=100k$ ,  $R_2=50k$ ,  $R_S=3k$ ,  $R_L=2k$ .

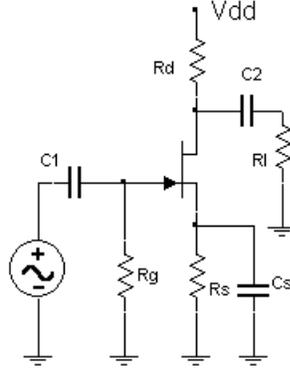


Circuit 1



Circuit 1

For circuit 2 top right,  $R_G=1M$ ,  $R_S=250$ ,  $R_D=1k$ ,  $R_L=2k$ .

For circuit 3 bottom,  $V_{EE}=-10V$ ,  $R_G=500k$ ,  $R_E=2k$ ,  $R_D=3k$ ,  $R_L=4k$ .

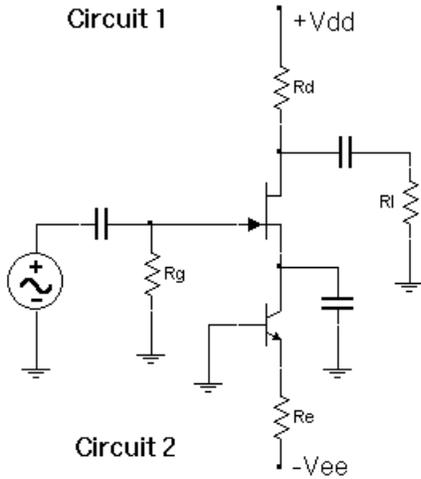

Circuit 2

## Answers

First, find  $g_{m0}$  for the device as it is the same for all three circuits.  $g_{m0} = -2 \cdot I_{DSS} / V_{GS(off)}$ .  
 $g_{m0} = -2 \cdot 16\text{mA} / -4\text{V} = 8\text{mS}$ .

### Circuit 1 top left, voltage divider bias, source follower.

$$Z_{in} = 100\text{k} || 50\text{k} = 33\text{k}$$

$$V_G = 30\text{V} \cdot 50\text{k} / (100\text{k} + 50\text{k}) = 10\text{V}$$

Assume  $V_{GS} = -2\text{V}$  (i.e.,  $1/2$  of  $V_{GS(off)}$ ) as a starting point.

$$\text{Therefore, } V_S = V_G - V_{GS} = 10\text{V} - (-2\text{V}) = 12\text{V}$$

$$\text{And, } I_D = I_S = V_S / R_S = 12\text{V} / 3\text{k} = 4\text{mA}$$

Crosscheck:  $I_D = I_{DSS} (1 - V_{GS} / V_{GS(off)})^2 = 16\text{mA} (1 - -2\text{V} / -4\text{V})^2 = 4\text{mA}$  The estimate was perfect. If not, adjust  $V_{GS}$  and try again until the two  $I_D$  calcs are the same.

$$g_m = g_{m0} \sqrt{I_D / I_{DSS}} = 8\text{mS} \sqrt{4\text{mA} / 16\text{mA}} = 4\text{mS}$$

$$A_v = g_m \cdot r_s / (1 + g_m \cdot r_s) \quad r_s = 3\text{k} || 2\text{k} = 1.2\text{k}$$

$$A_v = 4\text{mS} \cdot 1.2\text{k} / (1 + 4\text{mS} \cdot 2\text{k}) = .83$$

### Circuit 2 top right, self bias common source amplifier.

$$Z_{in} = 1\text{M}$$

Using a self bias graph,  $g_{m0} \cdot R_S = 8\text{mS} \cdot 250 = 2$ , which yields  $I_D / I_{DSS} = .38$

$$g_m = g_{m0} \sqrt{I_D / I_{DSS}} = 8\text{mS} \sqrt{.38} = 4.93\text{mS}$$

$$A_v = -g_m \cdot r_d \quad r_d = 1\text{k} || 2\text{k} = 667$$

$$A_v = -4.93\text{mS} \cdot 667 = -3.29$$

### Circuit 3 bottom, current source bias common source amplifier.

$$Z_{in} = 500\text{k}$$

$$I_d = (V_{EE} - 7\text{V}) / R_E = 9.3\text{V} / 2\text{k} = 4.65\text{mA}$$

$$g_m = g_{m0} \sqrt{I_D / I_{DSS}} = 8\text{mS} \sqrt{4.65\text{mA} / 16\text{mA}} = 4.31\text{mS}$$

$$A_v = -g_m \cdot r_d \quad r_d = 3\text{k} || 4\text{k} = 1.71\text{k}$$

$$A_v = -4.31\text{mS} \cdot 1.71\text{k} = -7.39$$