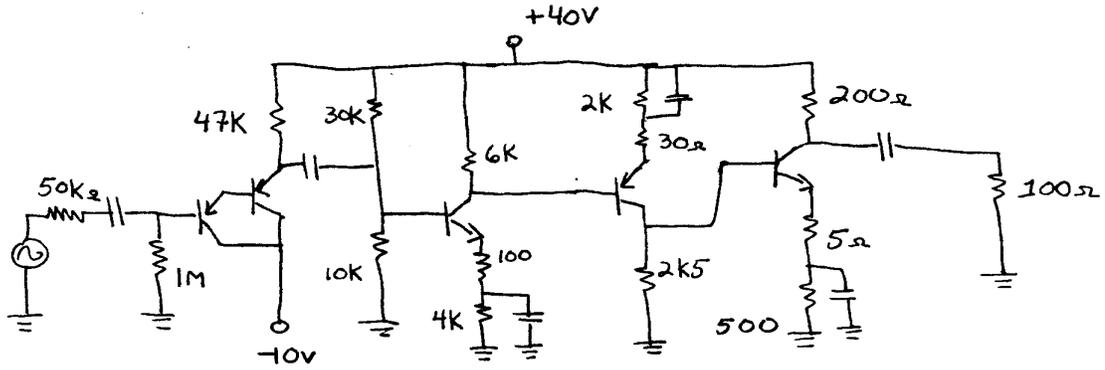


"MONSTERRIFIC" Problem # 1

LINEAR



$h_{fe} = 100$ each for the Darlington Pair, 200 for the remaining 3.
Find: Z_{in} of system, A_v of system.

To find Z_{in} and A_v , we need to find the $Z_{in(base)}$ and r'_e of each stage. This requires us to find I_E . Let's get this stuff out of the way first for later use.

$$I_{E_1} = \frac{40V - 1.4V}{47K} = .821mA \quad r'_{e_1} = 2 \cdot \frac{26mV}{.821mA} = 63.3\Omega$$

$$I_{E_2} = \frac{10V - .7V}{4K} = 2.27mA \quad r'_{e_2} = \frac{26mV}{2.27mA} = 11.5\Omega$$

$$I_{E_3} = \frac{40V - (26.4V + .7V)}{2K} = 6.35mA \quad (\text{note } V_{C_2} = V_{B_3} = 26.4V)$$

$$r'_{e_3} = \frac{26mV}{6.35mA} = 4.10\Omega$$

$$I_{E_4} = \frac{15.88V - .7V}{505\Omega} = 30.1mA \quad (\text{note } V_{C_3} = V_{B_4} = 15.88V)$$

$$r'_{e_4} = \frac{26mV}{30.1mA} = .864\Omega$$

$$Z_{in(base)4} = 200(5\Omega + .864) = 1K173\Omega$$

$$Z_{in(base)3} = 200(30\Omega + 4.10) = 6K82\Omega$$

$$Z_{in(base)2} = 200(100 + 11.5) = 22K3\Omega$$

$$Z_{in(base)1} = 100 \cdot 100 \left(63.3 + \underbrace{47K \parallel 10K \parallel 30K \parallel 22K3}_{5K01 = r_{E_1}} \right) = 50M73\Omega$$

CONTINUED.

NOTE THAT R_{E_1} is in parallel with the Biasing Resistors and $Z_{in}(\text{base})$ of stage 2. This is r_{E_1} .

Z_{in} of system.

this is equal to Z_{in1}

$$Z_{in1} = Z_{Bias} // Z_{in}(\text{base})_1 = 1M\Omega // 50M\Omega = \underline{981K\Omega}$$

NOTE: IGNORING r'_C of Darlington Pair

A_v of system

there are 5 gains to be considered, first of which is the input loading.

$$A_L = \frac{Z_{in}}{Z_{in} + R_s} = \frac{981K}{50K + 981K} = \underline{.952}$$

Note: $50K\Omega$ is quite high for a typical generator impedance, however this could easily represent the internal impedance of a high Z microphone. Note how the Darlington follower minimizes loss.

$$A_{v1} = \frac{r_{E_1}}{r'_{E_1} + r_{E_1}} = \frac{47K // 10K // 30K // 22K\Omega}{63.3\Omega + 47K // 10K // 30K // 22K\Omega} = \underline{.988}$$

$$A_{v2} = \frac{r_{C_2}}{r'_{C_2} + r_{E_2}} = \frac{6K // Z_{in}(\text{base})_3}{11.5 + 100} = \frac{3K19}{111.5} = \underline{28.6}$$

$$A_{v3} = \frac{r_{C_3}}{r'_{C_3} + r_{E_3}} = \frac{2K5 // Z_{in}(\text{base})_4}{30 + 4.1} = \frac{798\Omega}{34.1\Omega} = \underline{23.4}$$

$$A_{v4} = \frac{r_{C_4}}{r'_{C_4} + r_{E_4}} = \frac{200 // r_L}{1864 + 5} = \frac{66.7}{5.864} = \underline{11.4}$$

$$A_{vT} = A_L \cdot A_{v1} \cdot A_{v2} \cdot A_{v3} \cdot A_{v4} = .952 \cdot .988 \cdot 28.6 \cdot 23.4 \cdot 11.4 = \underline{7176}$$