

## Operational Amplifiers


## Practice Work Handout 1

Assume +/-15VDC supplies and  $A_{o1}=200,000$ .


1. Perform the conversions below.

$A_v = 40$	$A'_v =$	dB
$A'_v = -18$ dB	$A_v =$	
$P = .125$ Watts	$P' =$	dBW
$V' = -12$ dBV	$V =$	Volts

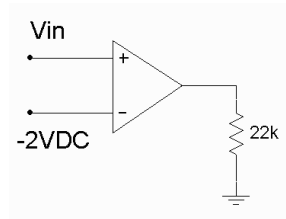
2. For the circuit below, sketch the output waveforms given inputs of +3VDC, 0VDC, and -5VDC.



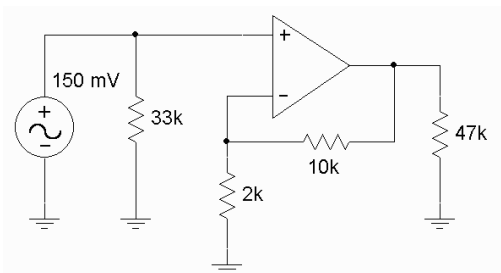3. Find the voltage gain, input impedance, and output voltage. If  $f_{\text{unity}}$  is 2 MHz, find  $f_2$ .



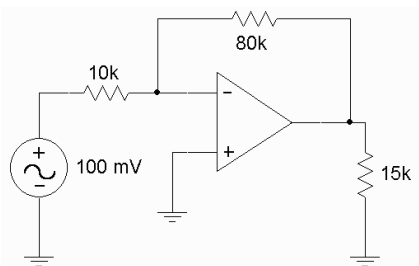4. For the circuit below, find the voltage gain, input impedance, and output voltage. If slew rate is 2 volts per microsecond, find  $f_{\text{max}}$  (power bandwidth) for a 10 volt peak output.



1. Perform the conversions below.

$$A'_v = 20 \cdot \log_{10} A_v = 32 \text{ dB (note this is } 2 \cdot 2 \cdot 10, \text{ or } 6\text{dB} + 6\text{dB} + 20\text{dB)}$$

$$A_v = 10^{(A'_v/20)} = .125 \text{ (the equation above, "backwards")}$$

$$P' = 10 \cdot \log_{10} (P/P_{\text{ref}}) \text{ (where dBW uses 1 W ref)} = -9 \text{ dBW}$$

$$\text{(or, } .5 \cdot .5 \cdot .5 \text{ which is } -3\text{dB} - 3\text{dB} - 3\text{dB)}$$

$$V = V_{\text{ref}} \cdot 10^{(V'/20)} \text{ (where ref = 1 Volt)} = .25 \text{ Volts}$$

$$\text{(or, } -6\text{dB} - 6\text{dB, which is } .5 \cdot .5 = .25)$$

2. Sketch the output waveforms given inputs of +3VDC, 0VDC, and -5VDC.

The reference is -2V so anything larger than this produces positive saturation (about +13 to +14VDC, for inputs one and two) while anything less than -2V produces negative saturation (about -13 to -14VDC, for input three).

3. Find the voltage gain, input impedance, and output voltage. If  $f_{\text{unity}}$  is 2 MHz, find  $f_2$ .

$Z_{\text{in}}$  is set by the 33k.

$$A_v = 1 + R_f/R_i = 1 + 10\text{k}/2\text{k} = 6.$$

$$f_2 = f_{\text{unity}}/A_{\text{noise}} = 2\text{MHz}/6 = 333\text{kHz. (note } A_n = A_v \text{ for this amplifier)}$$

4. Find the voltage gain, input impedance, and output voltage. If slew rate is 2 volts per microsecond, find  $f_{\text{max}}$  (power bandwidth) for a 10 volt peak output.

$Z_{\text{in}}$  is set by  $R_i = 10\text{k}$ .

$$A_v = -R_f/R_i = -80\text{k}/10\text{k} = -8.$$

$$V_{\text{out}} = V_{\text{in}} \cdot A_v = .1\text{V} \cdot (-8) = .8 \text{ volts inverted.}$$

$$f_{\text{max}} = \text{SR}/(2 \cdot \pi \cdot V_{\text{peak}}) = 2\text{E}6/(2 \cdot \pi \cdot 10\text{V}) = 31.8 \text{ kHz}$$

$$\text{(note } 2 \text{ V/uSec} = 2\text{E}6 \text{ V/Sec)}$$