
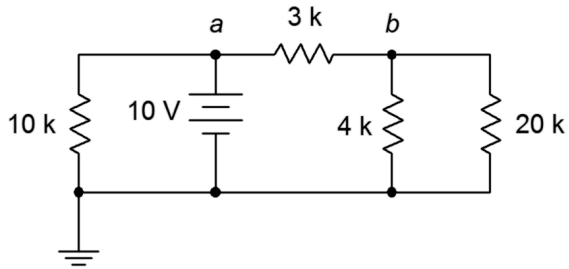


Answers are on the final pages

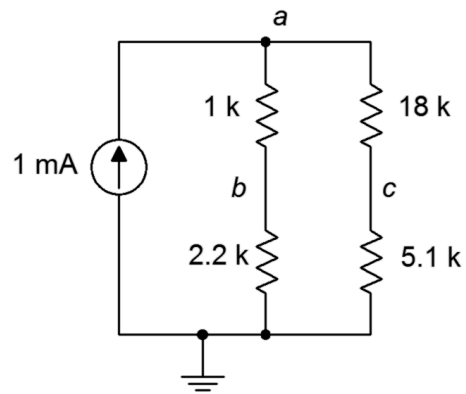
1. For the circuit below, find voltage  $V_{ab}$ . Also find the current through the 20 k.




2. For the circuit below, find voltage  $V_{bc}$ . Also find the current through the 1 k.



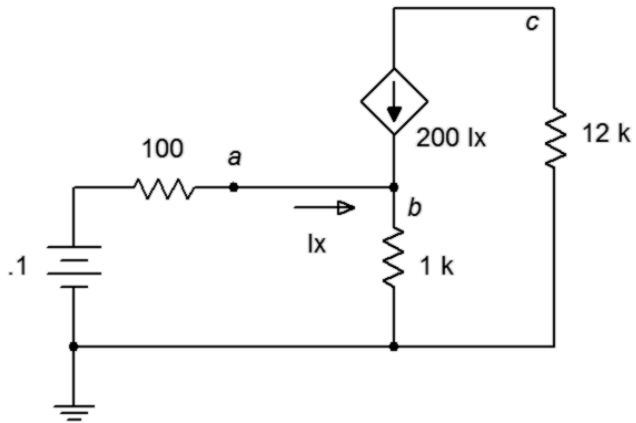3. For the circuit below, find the voltage across the 12 k.




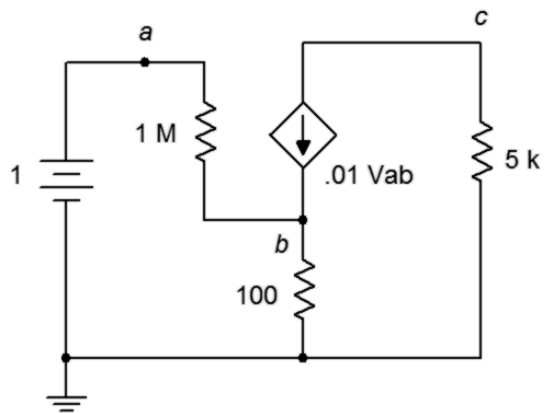4. For the circuit below, find the voltage across the 5 k.



## Answers

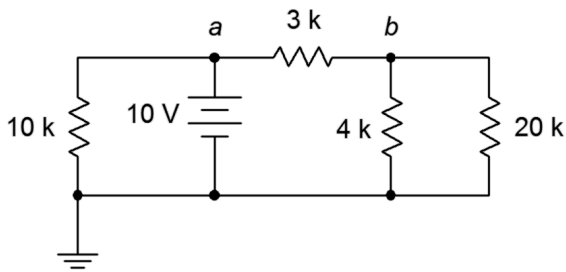1. For the circuit below, find voltage  $V_{ab}$ . Also find the current through the 20 k.



By definition,  $V_{ab} = V_a - V_b$ . By inspection,  $V_a = 10 \text{ V}$ .  $V_b$  may be found via a voltage divider between the 3 k and the 4 k || 20 k combo.  $4 \text{ k} || 20 \text{ k} = 3.333 \text{ k}$


$$V_b = 10 \text{ V} * 3.333 \text{ k} / (3.333 \text{ k} + 3 \text{ k}) = 5.263 \text{ V}$$

Thus,  $V_{ab} = 4.737 \text{ V}$

Knowing  $V_b$ , the current through the 20 k is found via Ohm's law.

$$I = V_b / 20 \text{ k} = 5.263 \text{ V} / 20 \text{ k} = .2631 \text{ mA}$$

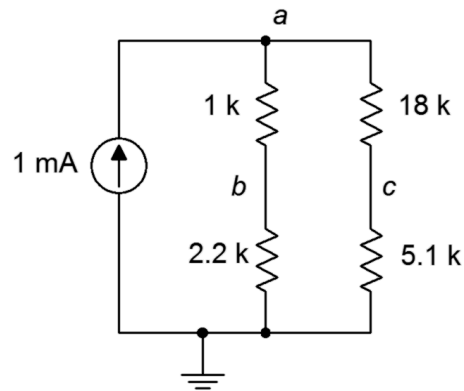2. For the circuit below, find voltage  $V_{bc}$ . Also find the current through the 1 k.



By definition,  $V_{bc} = V_b - V_c$ . These can be found via Ohm's law once the currents are known. The currents may be determined via current divider rule and KCL. Treat each series pair as a single resistance (3.2 k left, 23.1 k right)

$$I_{\text{left}} = 1 \text{ mA} * 23.1 \text{ k} / (23.1 \text{ k} + 3.2 \text{ k}) = .8783 \text{ mA} \text{ (I of 1 k, also)}$$


$$I_{\text{right}} = 1 \text{ mA} - .8783 \text{ mA} = .1217 \text{ mA}$$

$$V_b = .8783 \text{ mA} * 2.2 \text{ k} = 1.932 \text{ V}$$

$$V_c = .1217 \text{ mA} * 5.1 \text{ k} = .6207 \text{ V}$$

$$V_{bc} = 1.932 \text{ V} - .6207 \text{ V} = 1.311 \text{ V}$$

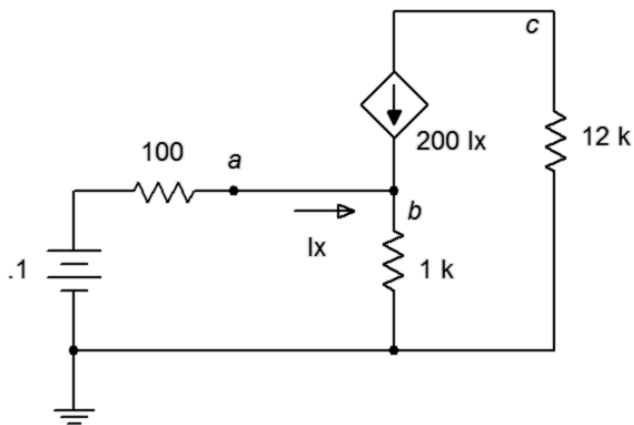3. For the circuit below, find the voltage across the 12 k.



Using nodal analysis, define the currents at node b.

$$I_x + 200I_x = I_{1k}$$

$I_x$  is the current flowing through point a. Also,  $V_a = V_b$ .

Further, note that  $I_x = (.1 - V_b)/100$ .

Expand:

$$201(.1 - V_b)/100 = V_b/1 \text{ k}$$

$$.201 = V_b(201/100 + 1/1 \text{ k})$$

$$V_b = 99.9502735 \text{ mV}$$

$$\text{Therefore } I_x = (100 \text{ mV} - 99.9502735 \text{ mV})/100 = .497265 \text{ uA}$$


$$\text{And finally, } V \text{ of } 12 \text{ k} = 12 \text{ k} * 200 * .497265 \text{ uA} = 1.193 \text{ V}$$

Crosschecking:  $I$  Of  $1 \text{ k} = V_b / 1 \text{ k} = 99.9502735 \text{ uA}$

$I_x + 200 * I_x = 99.950265 \text{ uA}$  so KCL checks within round-off error.

FYI: the circuit above is a simplified amplifier using a bipolar junction transistor. The amplification factor is approximately equal to the ratio the right and middle resistors.

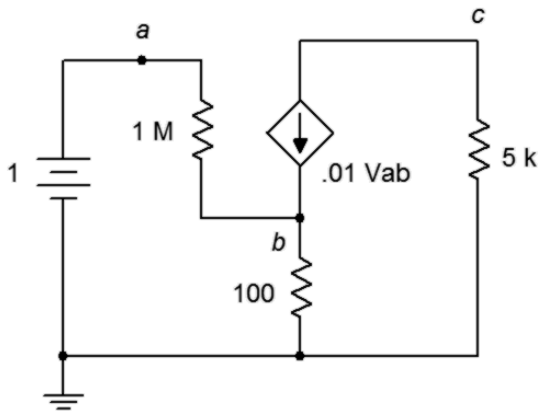4. For the circuit below, find the voltage across the 5 k.



Using nodal analysis, define the currents at node b.

$$I_{1M} + .01V_{ab} = I_{100}$$

Note that  $I_{1M} = (1-V_b)/1\text{ M}$ , and that  $V_{ab} = 1 - V_b$ .

Expand:

$$(1-V_b)/1\text{ M} + .01(1 - V_b) = V_b/100$$

$$1/1\text{ M} - V_b/1\text{ M} + .01 - .01V_b = V_b/100$$

$$.010001 = V_b(1/1\text{M} + .01 + 1/100)$$

$$V_b = .5200024999\text{ V}$$

$$\text{Therefore, } V_{ab} = 1\text{ V} - .500024999\text{ V} = .499975\text{ V}$$

$$\text{The VCCS} = .01 * .499975\text{ V} = 4.99975\text{ mA}$$

$$\text{Therefore, V of } 5\text{ k} = 24.999\text{ volts.}$$

You can also crosscheck KCL at node b but make sure that you leave many digits of precision because  $I_{1M}$  is very small compared to the other currents (roughly .5 uA).

FYI: This circuit is a simplified amplifier using an FET (field effect transistor). The amplification factor is approximately equal to the transconductance (here, .01) times the 5 k, the result then divided by the quantity 1 plus the product of transconductance times the 100 ohm. This works out to 25 for this circuit (i.e., 1 volt times 25 yields 25 volts).